
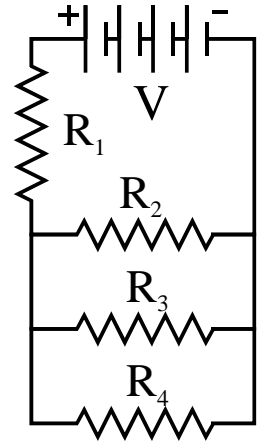

 
## Quiz 12:3D DC Circuits – Resistors in Series & Parallel [I-L]

A battery, which has an EMF of  $V = 12.0$  Volts, is connected in series with four resistors which have the following values:  $R_1 = 120 \Omega$ ,  $R_2 = 240 \Omega$ ,  $R_3 = 480 \Omega$  and  $R_4 = 60.0 \Omega$ .




1. What will be the total resistance of this circuit? [3 pts]
  
2. What will be the current flowing through resistor  $R_1$  in this circuit? [3 pts]



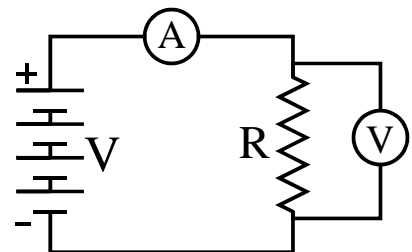3. You are looking for a resistor which has a value of  $1700 \Omega \pm 10\%$ . Fill in the blanks in the diagram of the resistor to the left that will give you the desired resistance. [3 pts]

A battery, which has an internal resistance of  $r = 1.50 \Omega$ , is connected to a load resistance of  $R = 8.5 \Omega$ . The resulting current flowing through the ammeter is measured to be  $I = 2.00$  Amperes.



4. What will be the reading on the voltmeter across the  $V$  load resistance? [3 pts]

5. What is the EMF of this battery? [3 pts]