

# PHYSICS HOMEWORK #146

# ELECTROSTATIC POTENTIAL CAPACITORS & CAPACITANCE

1. A given capacitor is rated to store 450  $\mu\text{C}$  of charge whenever a potential difference of 12.0 Volts is applied.
- What is the capacitance of this capacitor?
  - How much charge will this capacitor store when a potential difference of 72.0 Volts is applied?

$$C = \frac{q}{V} = \frac{\epsilon \cdot A}{d} \quad \epsilon = \epsilon_o \cdot K \quad \epsilon_o = 8.85 \cdot 10^{-12} \cdot \frac{\text{Farad}}{\text{m}}$$

2. What is the capacitance of capacitor which can store 720  $\mu\text{C}$  of charge whenever a potential difference of 45.0 Volts is applied?
3. How much charge can be stored in a capacitor rated at 210  $\mu\text{F}$ , if a potential difference of 6.00 Volts is applied?
4. How much charge can be stored in a 2000  $\mu\text{F}$  capacitor when a potential difference of 15.0 Volts is applied?
5. A parallel plate capacitor is made of two parallel plates, each of which has an area of 2.0  $\text{m}^2$ , and which are separated by 1.20 mm of air. What is the capacitance of this capacitor?
6. What will be the capacitance of a parallel plate capacitor which is made from two parallel plates, each with an area of 3.5  $\text{m}^2$ , which are separated by 0.85 mm of mica ?

<u>DIELECTRIC MATERIAL</u>	<u>DIELECTRIC CONSTANT K</u>
AIR	1.0
PARAFFIN	2.2
POLYETHYLENE	2.3
POLYSTYRENE	2.5
HARD RUBBER	2.8
MICA	6.0
GLASS	8.0

7. What will be the capacitance of a parallel plate capacitor consisting of two two parallel plates, each of which has an area of 13.3  $\text{m}^2$ , which are separated by 0.0145 mm of polystyrene?
8. A parallel plate capacitor is to be made from two conducting plates separated by 0.022 mm of polyethylene. This capacitor is to have a total capacitance of 220  $\mu\text{F}$ . What should the area of each plate of this capacitor be?
9. What will be the total capacitance if a 250  $\mu\text{F}$  capacitor is connected in parallel with a 150  $\mu\text{F}$  capacitor?
10. What will be the total capacitance if a 240  $\mu\text{F}$  capacitor is connected in series with a 440  $\mu\text{F}$  capacitor?
11. What will be the total capacitance if two 500  $\mu\text{F}$  capacitors are connected in series with each other but which are connected in parallel with a 250  $\mu\text{F}$  capacitor? See diagram at the right!


**Series**

$$\frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{C_t}$$

**Parallel**

$$C_1 + C_2 = C_t$$

**Energy**

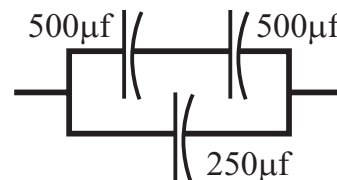


12. How much energy will be stored in a 420  $\mu\text{F}$  capacitor to which a potential difference of  $V = 12.0$  Volts has been applied?
13. How much energy would be stored in a 2000  $\mu\text{F}$  capacitor attached to a 120 Volt power supply?
14. A capacitor is rated at 1200  $\mu\text{F}$ . What potential difference should be applied to this capacitor so that the energy stored in this capacitor is 12.4 Joules?
15. What will be the total capacitance if a 350  $\mu\text{F}$ , a 520  $\mu\text{F}$  and a 700  $\mu\text{F}$  capacitor are all connected in series?

Answers to opposite side: 6. 9,400,000 Volts 7a.  $1.5 \times 10^5$  Volts b. 0.0 Volts c.  $-1.15 \times 10^6$  Volts d.  $4.77 \times 10^6$  Volts  
 7e.  $4.42 \times 10^6$  Volts 8a. 1.05 J b. 0.0 J c. -8.08 J d. 33.4 J e. 30.9 J 9a. -9.75 J b. -3.99 J c. -4.08 J  
 9d. -7.10 J e. 15.5 J 10a. B b. A c. E d. E

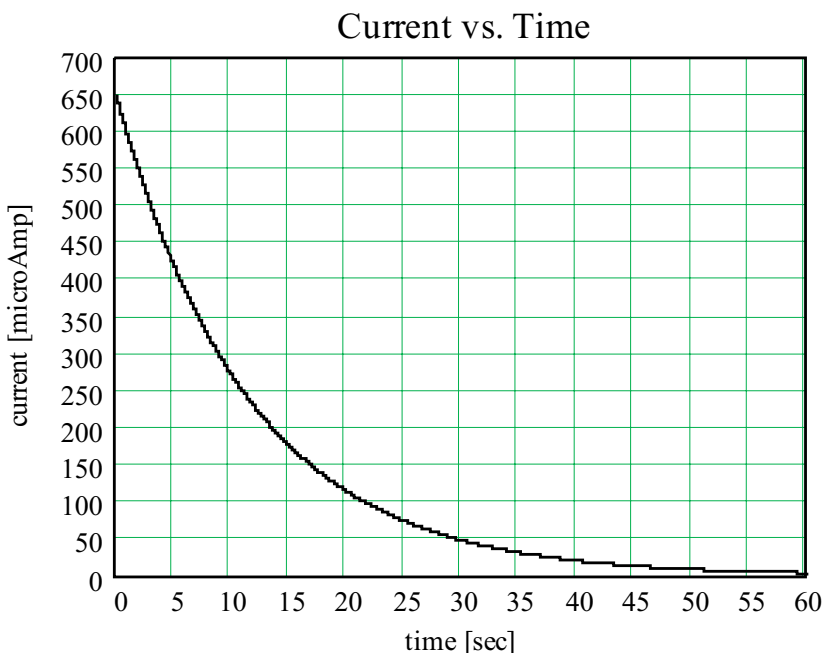16. A capacitor with a capacitance  $C$  is attached to a power supply which has a potential  $V$  and is then fully charged. This capacitor is then attached to a simple series circuit consisting of a galvanometer and a  $13,000 \Omega$  resistor. The graph to the right represents the current flowing out of this capacitor as a function of time through the galvanometer.

- What was the initial current flowing out of the capacitor?
- What was the initial voltage across the capacitor?
- What is the time constant for this circuit?
- Write an equation describing the current flowing out of this circuit as a function of time?
- Using the equation derived in d above predict the current flowing out of this capacitor after  $t = 30$  seconds and compare to the value on the graph.
- What was the total charge contained in this capacitor?
- What is the capacitance of this capacitor?
- How much charge will be stored in this capacitor after  $t = 20$  seconds?
- What will be the current flowing out of this capacitor after  $t = 85$  seconds?



17. A capacitor, which has a capacitance of  $470 \mu\text{F}$ , is attached to a  $6.00$  Volt battery and is fully charged. This capacitor is then removed from the battery and is attached in series to a  $1500 \Omega$  resistor.

- What is the time constant for this circuit?
- What will be the total charge stored in this capacitor?
- What will be the initial current flowing through this circuit?
- What will be the current flowing through this circuit after  $1.5$  seconds?
- How long will it take for the current flowing in this circuit to fall to  $1\%$  of its initial value?

18. A  $220 \mu\text{F}$  capacitor is charged up by a  $12.0$  Volt battery.

- What will be the charge stored on this capacitor after being charged up?

**This capacitor is then attached to a second capacitor, which is initially uncharged and has a capacitance of  $470 \mu\text{F}$ .**

- What will be the total charge stored on both of these capacitors after being attached together?
- What will be the charge stored on each of these capacitors after being attached together?
- What will be the potential difference across each of these capacitors after being attached together?

**ANSWERS TO THE OPPOSITE SIDE:**

19a..  $5000 \mu\text{C}$ ,  $19,800 \mu\text{C}$    b.  $24,800 \mu\text{C}$    c.  $7750 \mu\text{C}$ ,  $17,050 \mu\text{C}$    d.  $7.75$  Volts   e.  $14,800 \mu\text{C}$    f.  $4625 \mu\text{C}$ ,  
 19f.  $10,175 \mu\text{C}$    g.  $4.625$  Volts   20a.  $3300 \mu\text{C}$ ,  $24,750 \mu\text{C}$    b.  $28,050 \mu\text{C}$    c.  $7010 \mu\text{C}$ ,  $21,040 \mu\text{C}$   
 20d.  $12.75$  Volts   e.  $21,450 \mu\text{C}$    f.  $5360 \mu\text{C}$ ,  $16,100 \mu\text{C}$    g.  $9.75$  Volts   21a.  $2.30 \mu\text{F}$    b.  $27.6 \mu\text{C}$    c.  $166 \mu\text{J}$   
 21d.  $13.8 \mu\text{F}$    e.  $166 \mu\text{C}$    f.  $994 \mu\text{J}$    g.  $828 \mu\text{J}$    22.  $48.0 \text{ C}$

19. A 1000  $\mu\text{F}$  capacitor is charged up by a 5.00 Volt battery while a second capacitor, which has a capacitance of 2200  $\mu\text{F}$  is charged up with a 9.00 Volt battery.
- What will be the charge stored on each capacitor after being charged up?
- These capacitors are then attached together, positive to positive, negative to negative.**
- What will be the total charge stored on these two capacitors after being attached together?
  - What will be the charge stored on each capacitor after being attached together?
  - What will be the potential difference across each of the these capacitors after being attached together?
- Suppose instead that these two capacitors had been connected together, positive to negative, positive to negative.**
- What will be the total charge stored on these two capacitors after being attached together?
  - What will be the charge stored on each capacitor after being attached together?
  - What will be the potential difference across each of the these capacitors after being attached together?
20. A  $C_1 = 550 \mu\text{F}$  capacitor is charged up by a  $V_1 = 6.00$  Volt battery while a second capacitor, which has a capacitance of  $C_2 = 1650 \mu\text{F}$  is charged up with a  $V_2 = 15.0$  Volt battery.
- How much charge will be stored on each capacitor after being charged by their respective batteries?
- These two capacitors are then attached together, positive to positive, negative to negative.**
- What will be the total charge stored on these two capacitors after being attached together?
  - What will be the charge stored on each capacitor after being attached together?
  - What will be the potential difference across each of the these capacitors after being attached together?
- Suppose instead that these two capacitors had been connected together, positive to negative, positive to negative.**
- What will be the total charge stored on these two capacitors after being attached together?
  - What will be the charge stored on each capacitor after being attached together?
  - What will be the potential difference across each of the these capacitors after being attached together?
21. A parallel plate capacitor is made up of two plates, each of which has an area of  $6.50 \text{ m}^2$ , separated by  $0.0250 \text{ mm}$  of air.
- What will be the capacitance of this capacitor?
  - How much charge will be stored in this capacitor when charged to a potential of 12.0 Volts?
  - How much energy will be stored in this capacitor when charged up to a potential of 12.0 Volts?
- Suppose that the air between the plates is replaced by mica. [K = 6.0]**
- What will be the new capacitance of this capacitor?
  - How much charge will be stored in this capacitor when charged to a potential of 12.0 Volts?
  - How much energy will be stored in this capacitor when charged up to a potential of 12.0 Volts?
- Suppose that you now attempt to remove the mica from the capacitor.**
- How much work would be required to remove the mica?
22. A parallel plate capacitor is made of two parallel plates, each with an area  $A$ , separated by a distance  $d$  and which is filled with air. This capacitor has a capacitance  $C$ . Suppose that this capacitor is changed so that the **area** of each plate is **tripled**, the **distance** between the plates is **halved** and the air is replaced with **glass**, which has a dielectric constant of  $K = 8.00$ . What is the new capacitance of this capacitor?

Answers to opposite side: 16a. $650 \mu\text{A}$				b. 8.45 Volts		c. 11.5 s		d. $I = I_0 \cdot e^{-t/\tau} = 650 \mu\text{A} \cdot e^{-t/11.5}$	
16e. $48.0 \mu\text{A}$		f. $7475 \mu\text{C}$		g. $885 \mu\text{F}$		h. $1300 \mu\text{C}$		i. $0.40 \mu\text{A}$	
17d. $476 \mu\text{A}$		e. 3.25 s		18a. $2640 \mu\text{C}$		b. $2640 \mu\text{C}$		c. $1800 \mu\text{C}, 840 \mu\text{C}$	
								d. 3.82 Volts	

CAPACITORS AND CAPACITIVE REACTANCE

1. Consider a capacitor consisting of two parallel plates, each with an area of 2.35 meters<sup>2</sup>, separated by a distance of d = 0.0025 millimeters. Initially, this capacitor is uncharged and at t = 0 seconds it is connected in series with a resistance of 450 Ω and a battery which has an EMF of 12.0 Volts.
  - a. What is the capacitance of this capacitor?
  - b. What will be the initial current flowing through this circuit?
  - c. What will be the initial voltage drop across the resistor?
  - d. What will be the initial voltage drop across the capacitor?
  - e. What will be the current flowing in this circuit a long time after it has been connected?
  - f. What will be the voltage drop across the resistor a long time after this circuit has been connected?
  - g. What will be the voltage drop across the capacitor a long time after the circuit has been connected?
  - h. What is the time constant for this circuit?
  - i. Write an equation describing the current flowing through this circuit as a function of time?
  - j. What will be the current flowing through this circuit t = 2.00 milliseconds after it has been connected?
  - k. How much charge will be stored in this capacitor t = 2.00 milliseconds after it has been connected?

**Suppose now that the V = 12.0 Volt battery is removed and is replaced by an**

**AC power supply of V<sub>p</sub> = 170 Volts at a frequency of f = 320 Hz.**

- l. What will be the **capacitive reactance** of this circuit?
- m. What will be the **RMS** current flowing through this circuit?
- n. What will be the **phase angle** in this circuit?
- o. What will be the **power factor** in this circuit?
- p. At what rate is **energy** being consumed in this circuit?

$$X_c = \frac{1}{\omega C}$$

$$Z = \sqrt{R^2 + (X_L - X_c)^2}$$

$$\cos(\phi) = \frac{R}{Z}$$

2. Consider a capacitor consisting of two parallel plates, each with an area of 4.25 meters<sup>2</sup>, separated by a distance of d = 0.00130 millimeters. Initially, this capacitor is connected in series with a 25,000 Ω resistor and a V = 15.0 Volt DC power supply until the capacitor is fully charged.
  - a. What is the capacitance of this capacitor?
  - b. What will be the current flowing through this circuit after the capacitor has been fully charged?
  - c. What will be the voltage drop across the resistor after the capacitor has been fully charged?
  - d. What will be the voltage drop across the capacitor after the capacitor has been fully charged?

**This circuit is then removed from the battery and the two leads are shorted together to form a simple circuit consisting of a capacitor and resistor in series.**

- e. What will be the time constant for this circuit?
- f. What will be the current flowing in this circuit immediately after it has been connected?
- g. What will be the voltage drop across the resistor a long time after this circuit has been connected?
- h. What will be the voltage drop across the capacitor a long time after the circuit has been connected?
- i. Write an equation describing the current flowing through this circuit as a function of time?
- j. What will be the current flowing through this circuit 0.3 seconds after this circuit has been connected?
- k. How much charge will remain in this capacitor 0.3 seconds after this circuit has been connected?

**The resistor and capacitor in series are now connected to an AC power supply which has a voltage of V<sub>p</sub> = 45.0 Volts at a frequency of f = 1.20 Hz.**

- l. What is the capacitive reactance of this capacitor at this frequency?
- m. What will be the impedance of this circuit?
- n. At what rate will energy be dissipated in this circuit?

Answers to opposite side: 3a. 44.8 Ω   b. 1.51 Ω   c. 50.0 Ω   d. 31.8 Volts   e. 0.900 Amps   f. 0.64 Amps  
3g. 60.0°   h. 50.0 %   i. 10.1 Watts   k. 80.7 Hz.   l. 8.22 Ω   m. 8.22 Ω   n. 25.0 Ω   o. 100 %   p. 40.7 Watts